

IA Circuits


No. 1

Date 31.12.18

- charge in an electric field experiences $\vec{F} = q\vec{E}$
- In a wire: $I = \frac{dQ}{dt} = nqA \langle v \rangle$ cross sectional area.
- p.d is work done per unit charge, in moving q in \vec{E} .
- emf \mathcal{E} is the energy gained per unit charge in a cell.

- ~~Kirchoff~~ Kirchhoff's current law: current conserved at junction
- Kirchhoff's voltage law: around any loop, $\sum V_i = 0$ (for cons energy).

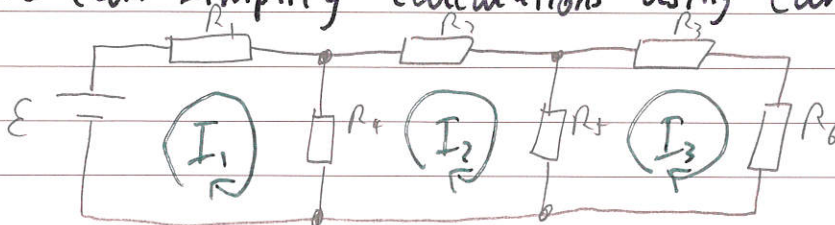We can simplify calculations using current loops:



$$\therefore \mathcal{E} - I_1 R_1 - (I_1 - I_2) R_4 = 0, \quad -I_2 R_2 - (I_2 - I_3) R_5 - (I_2 - I_1) R_4 = 0$$

... (3 eq with 3 unknowns).


- For voltage, we can arbitrarily label voltage w.r.t any reference point of our choosing (negative terminal usually).

Capacitors

Defined by $C = \frac{Q}{V}$. $\therefore W = Vdq = \frac{1}{2} CV^2$


In an RC circuit with a charged capacitor:
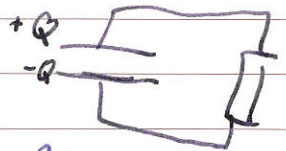
$$V = IR = \frac{Q}{C} \quad \therefore \frac{dQ}{dt} = \frac{Q}{RC} \Rightarrow Q(t) = Q_0 e^{-\frac{t}{RC}}$$



\hookrightarrow exponential decay with characteristic time $\tau = RC$

To charge a cap

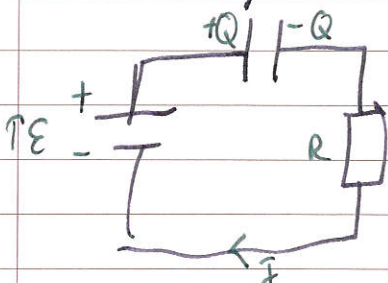

$$\mathcal{E} = IR + \frac{Q}{C}$$

$$\Rightarrow Q = C\mathcal{E}(1 - e^{-\frac{t}{RC}})$$


Inductors

$$\mathcal{E} = - \frac{d\phi_B}{dt}$$

But we also have $\phi_B = LI$ by definition.
↑
self-inductance.

$$\therefore \mathcal{E} = -L \frac{dI}{dt}$$

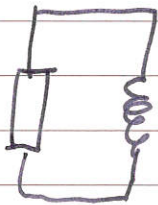↳ stores energy in the field: $w = \frac{1}{2} LI^2$



In an RL circuit, $-IR - L \frac{dI}{dt} = 0$

$$\Rightarrow I(t) = I(0) e^{-\frac{tR}{L}}$$

i.e. exponential decay with characteristic $\tau = \frac{L}{R}$.